

5 Register multiplication

Saturday, 15 February 2025 22:27

Implement additional instructions and/or hardware that can speed up EEP1 register multiplication. Limited to using no more than 64 full adders. (8 Issie adder blocks of 8 bits each)

Credit gained from:

- Solution
- Speed of solution in clock cycles, and its cost in hardware adders, with the "pure software" implementation in Lab 2
- Knowing how your solution can be used in different contexts: for example, to implement signed and unsigned multiplication

To speed up EEP1 multiplication, this requires the definition of **additional ALU instruction in the ISA**. This is possible because some combination of bits in the machine work are not currently used. Specifically the MOV instruction does not use register C, the 3 bits specifying this are set to 0 for a normal MOV.

There are 7 **additional** MOV instructions, using machine code as for MOV with nonzero in the C register field INS(4:2) can be used. The assembler recognises MOV_Cn Ra Rb where n = 1..7 and generates the correct machine code. You may use any of these instructions in Lab 2 to interface with additional hardware. For example MOV_C1 Ra, Rb could be used to implement Ra := Ra op Rb, where op is some new operation you have defined

5.2 Design Notes

Speeding up EEP1 multiplication requires the definition of **additional ALU instructions in the ISA**. This is possible because some combinations of bits in the machine work are not currently used. Specifically the MOV instruction does not use register C, the three bits specifying this are set to 0 for a normal MOV.

5.2.1 Implementing unused instructions

There are 7 **additional** MOV instructions, using machine code as for MOV with with nonzero in the c register field INS(4:2, can be used. The assembler recognises MOV_Cn Ra Rb where n = 1..7 and generates the correct machine code. You may use any of these instructions in Lab 2 to interface with additional hardware. For example MOV_C1 Ra, Rb could be used to implement Ra := Ra op Rb, where op is some new operation you have defined.

		ALUOPC	INS[8]=0	INS[8]=1	
		0	MOV ¹ Ra, Rb	MOV Ra, #IMM	
		1	ADD Rc, Ra, Rb	ADD Ra, #IMM	
		2	SUB Rc, Ra, Rb	SUB Ra, #IMM	
		3	ADC Rc, Ra, Rb	ADC Ra, #IMM	
		4	SBC Rc, Ra, Rb	SBC Ra, #IMM	
		5	AND Rc, Ra, Rb	AND Ra, #IMM	
		6	CMPI ¹ Ra, Rb	CMP Ra, #IMM	
		7	Shift Ra, Rb, #SCNT (see SHIFTOPC for Shift)		
¹ Instruction does not use Rc, this field is (0)					


Legend	Meaning
Imm4	4 bit unsigned immediate
Imm8	8 bit signed immediate
(0)	Must be 0 for current instructions, non-zero values are reserved for expansion

SHIFTOPC(1:0)	Shift
0	LSL
1	LSR
2	ASR
3	XSR

EEP1 machine code	INS bit	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
ALU	0	ALUOPC=7				a			Shift-opc(1)		b		Shift-opc(0)				
		ALUOPC=0..6				a			0		b		c				
									1			Imm8 (IMM)				(0)	


Conditions to implement the extra instruction:
8th bit of the machine code must be equal to 0 to be able to use register C field or else we would overlap with immediate operand

DPDECODE sheet

 

New logic:

 The NOT gate is connected to the 8th bit bus selector at the top



New logic:

The NOT gate is connected to the 8th bit bus selector at the top. Therefore when bit 8 = 0, we assert 0 into the DEMUX and use INS(4:2) as our field C to select the MOV_Cn operation

In this case I have selected MOV_C1 to be the operation to perform our multiplication

5.2.2 Adding to the datapath hardware


You can implement additional logic in and outputs from DPDECODE to control additional MUXes in the datapath. These MUXes can (only for the MOV_Cn instructions you decide to implement) select the output of your hardware block(s) instead of the ALU. You can put your hardware on a separate sheet which you add as a component to the datapath sheet.

Use hierarchy to simplify your hardware design (this will also speed up design and testing!). As an example, look at the **shift** block you are given as part of EEP1. Be creative: you do not have to follow the examples

4

in the notes exactly. Reuse hardware whenever possible when two different and related operations need to be implemented.

DATAPATH sheet

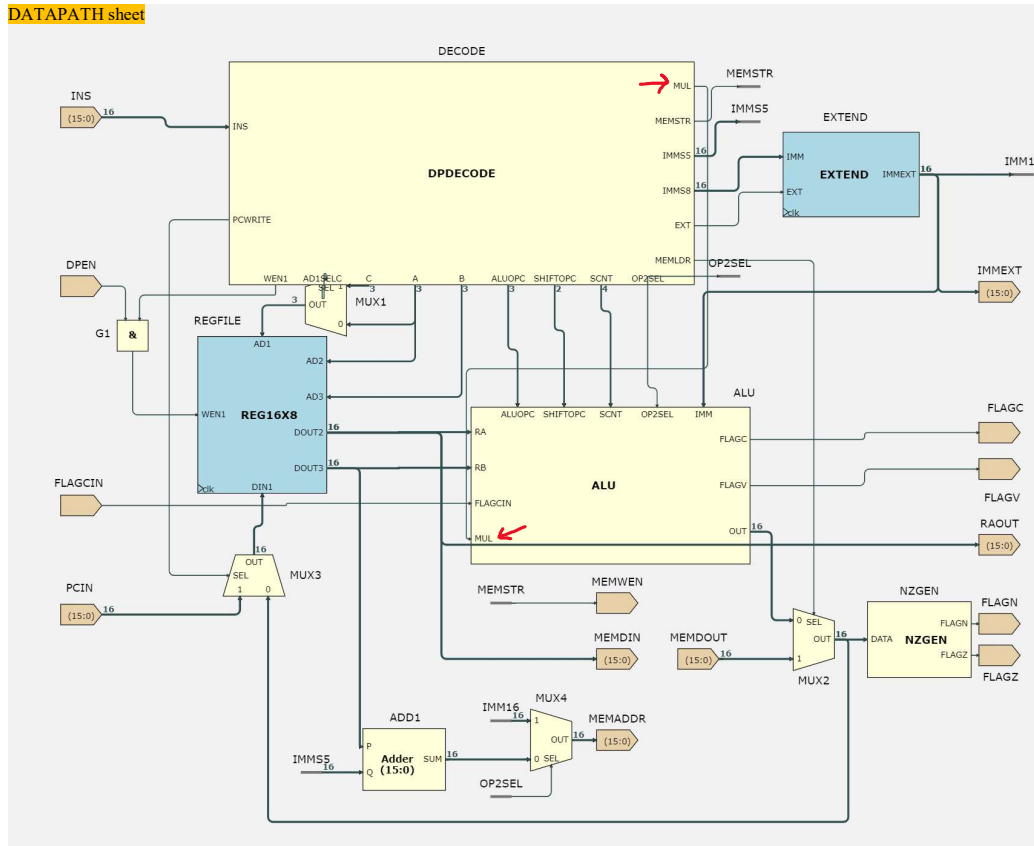


New:

Connection between MUL output and input of DPDECODE block and ALU block

5.2.3 Using your new hardware


Try to work out optimal sequences of instructions. Consider whether slightly different hardware could speed up the software.

ADD8 sheet

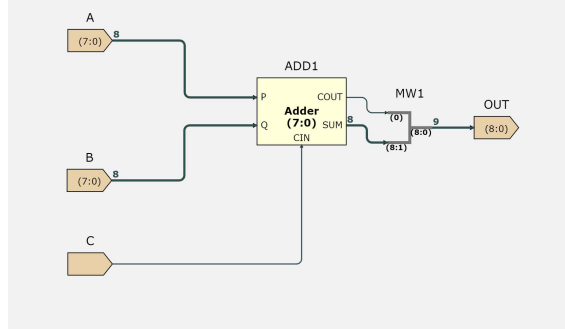


Note:
LSB of the 9 bit output is the carry out bit from the 8 bit adder

RIPPLE16 sheet

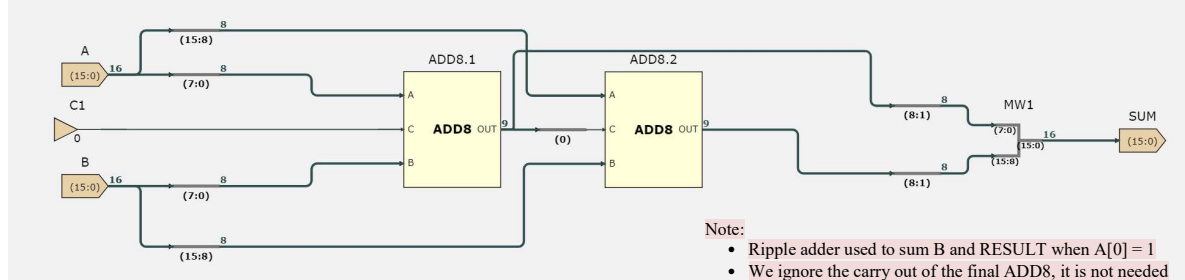

Note:
 • Ripple adder used to sum B and RESULT when A[0] = 1
 • We ignore the carry out of the final ADD8, it is not needed

MULT8 sheet

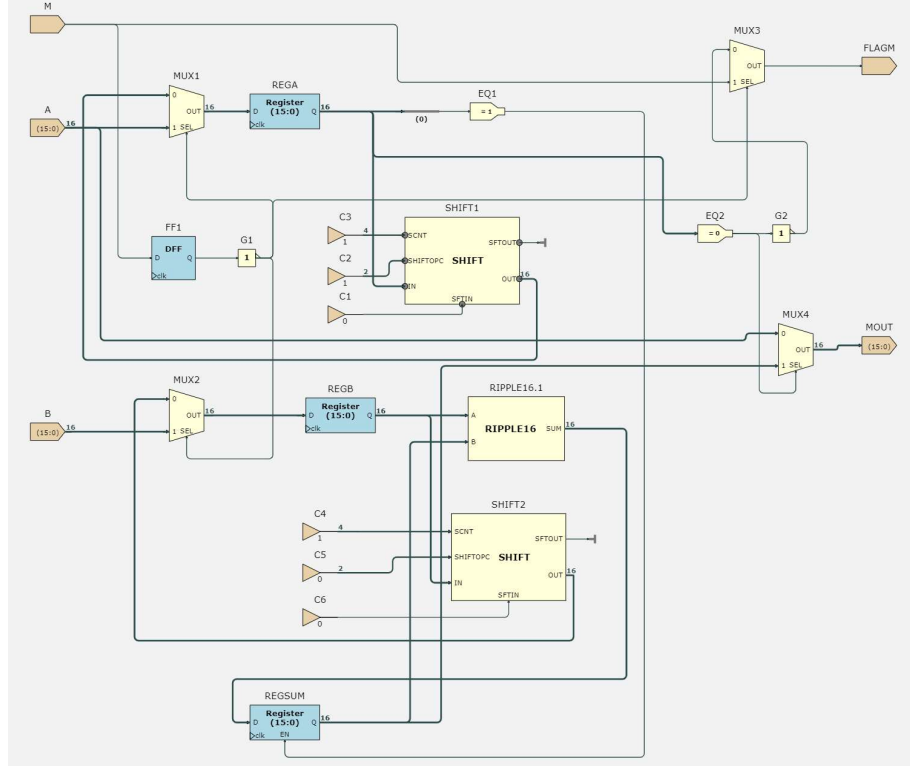

Note:
Implemented "Russian Peasant Multiplication" method via hardware. This is for 8 bit multiplication.

MUX1 and MUX2 help with initialising the register at the beginning, then we pass through the output of the register after the first clock

SHIFT1 = LSR
SHIFT2 = LSL


Bus comparator EQ1 acts as an enable for writing to the SUM register. Only when value A is odd will we write into the SUM register the sum of B and SUM

This implementation works for both signed and unsigned multiplication, however it takes longer for signed multiplication as we have to wait till A has been shifted all the way to 0x0000 from 0xFFXX


MUX3 ensures that FLAGM is not one clock cycle behind MUL so that we are able to stall PC immediately

FlagM = 1 (Multiplication is operating, therefore stall PC)
FlagM = 0 (Multiplication is not operating)

ALU sheet

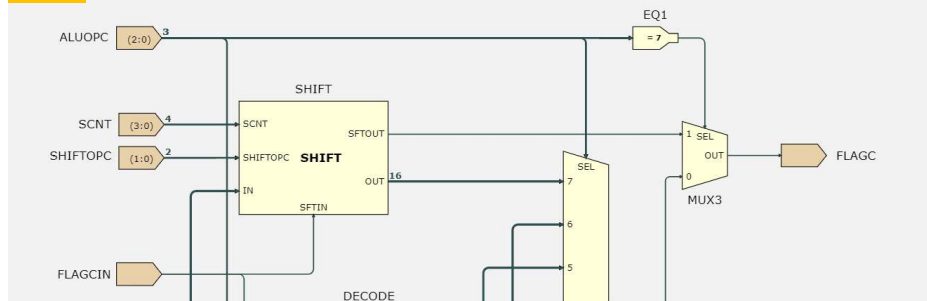

New:

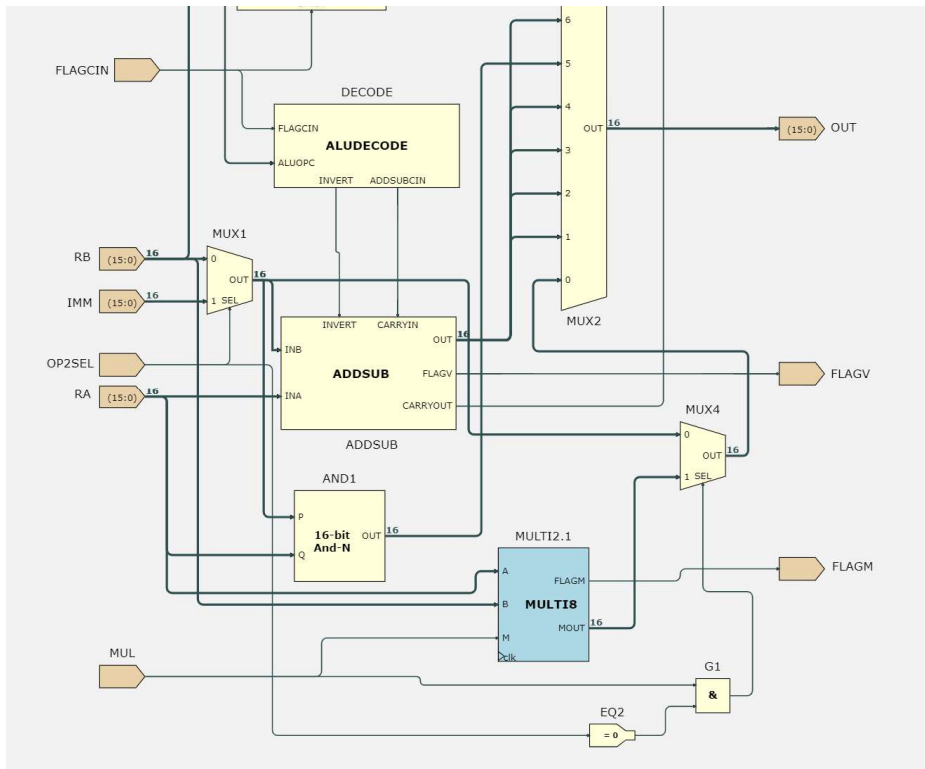

New:

An additional MUX (MUX4 in sheet)

Only the result of other multiplication is returned to terminal 0 of MUX2, depending if MUL is asserted or not.

- MUL = 1 - Multiplication is enabled

To differentiate between using the immediate or the multiplication operation, we need the bus comparator on OP2SEL to ensure it is 00 and MUL is asserted to select our multiplication output

Testing of new multiplication hardware (8 bit multiplication):

```

Lab2Challenge.txt
Lab2Challenge.ram
File Edit View

// UNSIGNED MULTIPLICATION (QUICK)
MOV R0, #3
MOV R1, #2
MOVC1 R0, R1

// END
MOV R0, #5
  
```

Simulating: eep1

Configure

Instructions

EndSimulation

Select Waves

Select RAM

	0	1	2	3	4	5	6	7	8	9	0
CONTROL.PATH.PCV(15:0)	x0000	x0001	x0002		x0002	x0003	x0004	x0005	x0006		x0000
Datapath.R0(15:0)	x0000	x0003	x0000	x0000	x0006	x0005		x0005	x0000		
Datapath.R1(15:0)	x0000	x0002							x0002	x0000	

Takes 4 clock cycles to execute multiplication

Limitation of implementation:

- There is rubbish value (0x0000) while computing the multiplication
- Number of clock cycles needed for operation is highly dependent on the values used

```

Lab2Challenge.txt
Lab2Challenge.ram
File Edit View

// UNSIGNED MULTIPLICATION (WORST CASE)
MOV R0, #255
MOV R1, #64
MOVC1 R0, R1

// END
MOV R0, #5
  
```

Simulating: eep1

Configure


Instructions

EndSimulation

Select Waves

Select RAM

	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	4
CONTROL.PATH.PCV(15:0)	x0001	x0002																	x0002	x0003	x0002
Datapath.R0(15:0)		xFFFF	x0000																x0000	xFFFF	x0000
Datapath.R1(15:0)		x0000	x0040																x0000	xFFFF	x0000
Datapath.G1 Out																					
Datapath.MUX1 Out	1	0																	0	0	
Datapath.ALU Out(15:0)	x0040	x0000																	x0000	xFFFF	x0000
Datapath.MUX4 Sel																					1

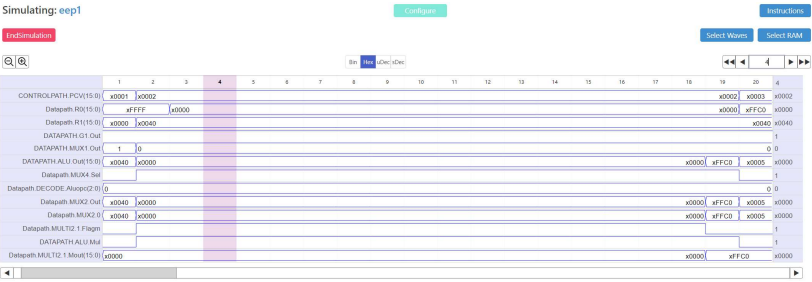

9 cycles to execute multiplication in worst case (where Ra needs to shift all 8 bits to complete operation)